

TRANSMISSION LINES SOLVED EXAMPLES

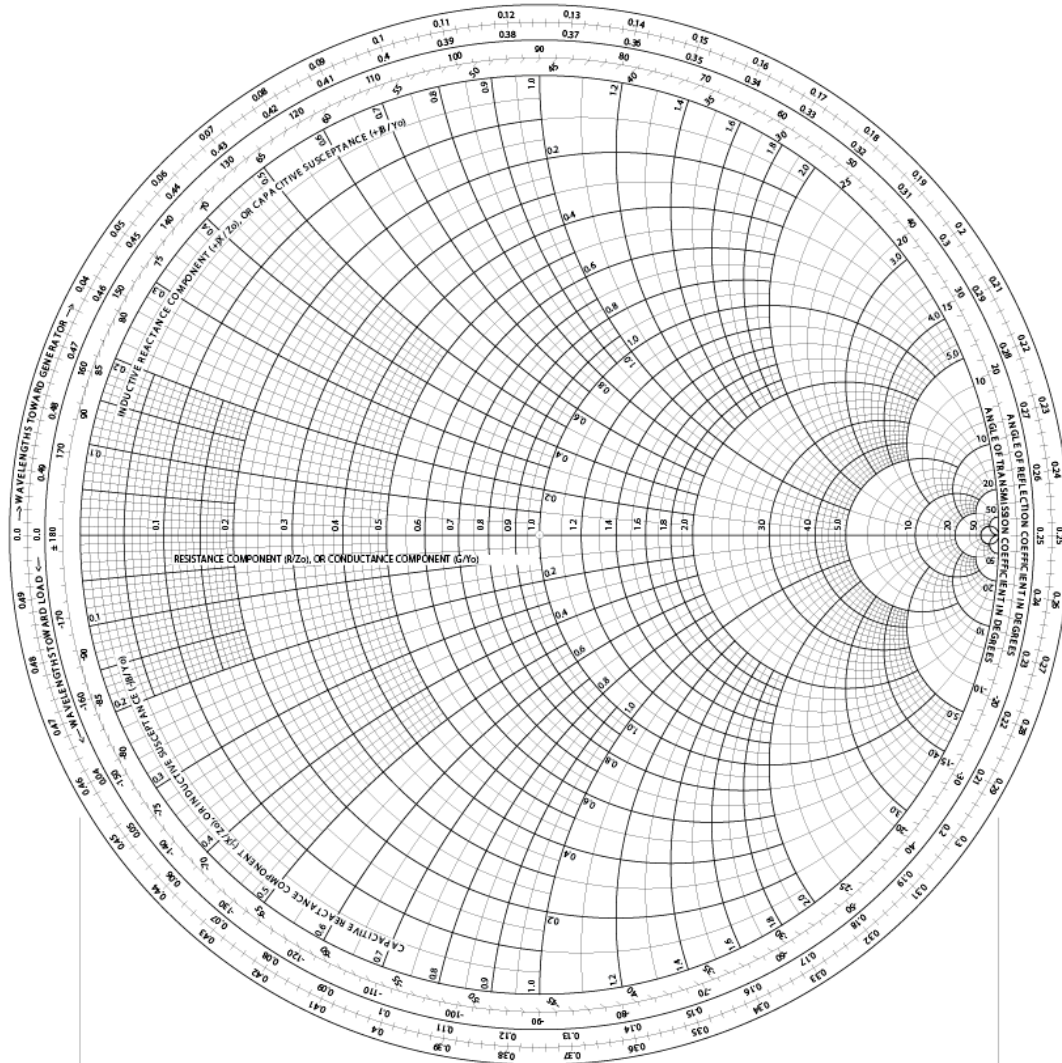


Table of contents


1. Impedances in Series	4
1.1 By calculation.....	4
1.2 Using Smith Chart	4
2. Impedances in Parallel.....	5
2.1 By calculation.....	5
2.2 Using Smith Chart	5
3. Lossless transmission line, terminated with an arbitrary impedance.....	6
3.1 Example:	6
3.2 By calculation.....	7
3.3 Using Smith Chart	10
4. Distance to first voltage maximum and minimum	11
5. Impedance matching	11
5.1 Shunt-series L-Network, by calculation	11
5.1.1 Example: Match load	14
5.2 Series shunt- L-Network, by calculation	15
5.2.1 Example: Match load	16
5.2.2 Example: Match load	17
5.2.3 Example: Match load	18
5.3 Shorted parallel stub as tuning element	19
5.4 Open series stub as tuning element.....	21
6. Lossy transmission line terminated with an arbitrary impedance	22
6.1 Example:	26
7. Half-wave transmission line impedance transformer	31
7.1 Example	33

Kuva 1: Impedances in Series.....	4
Kuva 2: Impedances in Parallel	6
Kuva 3: Transmission line.....	10
Kuva 4: Radially scaled parameters, SWR, Return Loss, Reflection Coefficient	11
Kuva 5: L-network matching	12
Kuva 6: Allowable Load impedance area for shunt-series network in Smith Chart representation	14
Kuva 7: Allowable Load impedance area for series -shunt -network in Smith Chart representation	16
Kuva 8 Allowable Load impedance area for capacitors only-network in Smith Chart representation	17
Kuva 9 Allowable Load impedance area for inductors only-network in Smith Chart representation.....	18
Kuva 10: Half-wavelength 1:4 impedance transformer.....	31
Kuva 11: Half-wavelength impedance transformer, schematic.....	31
Kuva 12: Half-wavelength impedance transformer, lumped model	32
Kuva 13: Voltage along t-line	35
Kuva 14: Current along t-line	35

Kaava 1.....	7
Kaava 2.....	13
Kaava 3.....	13
Kaava 4.....	15
Kaava 5.....	15
Kaava 6: Length of transmission line in shorted stub matching	20
Kaava 7: Length of shorted stub in shorted stub matching	20
Kaava 8: Propagation constant	22
Kaava 9: Speed of propagation	22
Kaava 10: Characteristic impedance of a lossy transmission line.....	23
Kaava 11: Voltage of a lossy transmission line as function of distance	24
Kaava 12: Current of a lossy transmission line as function of distance	24
Kaava 13: Input impedance of a lossy transmission line	25
Kaava 14: Power supplied by the generator.....	25
Kaava 15: Power transmitted to load	25
Kaava 16: Voltage reflection coefficient at load	26
Kaava 17: Voltage standing wave ratio	26

1. Impedances in Series

Example: Find Z_{IN}

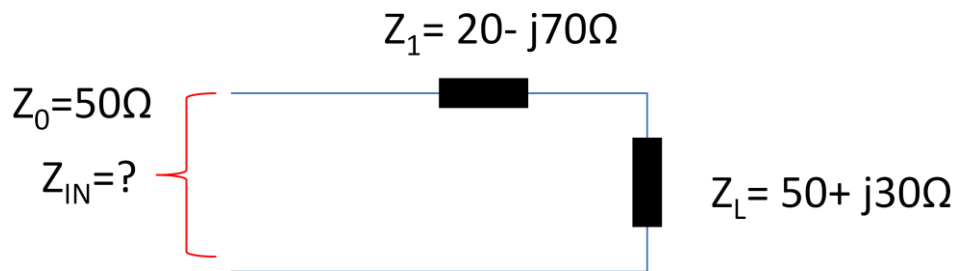


1.1 By calculation

$$Z_{IN} = Z_1 + Z_L = (20 - j70)\Omega + (50 + j30)\Omega = (70 - j40)\Omega = 80.6 \angle -29.7^\circ \Omega.$$

1.2 Using Smith Chart


- Normalize ; $Z_L' = Z_L/50$, $Z_1' = Z_1/50$,
- $Z_L' = 1 + j0.6\Omega \rightarrow$ find point on the Smith chart.
- $Z_1' = 0.4 - j1.4\Omega$ (resistance and capacitance in series)
 - o on a constant resistance circle, from Z_L' , rotate counterclockwise 1.4 units to add series C
 - o on a constant reactance arc, move 0.4 units to add a series R
- Convert back to system impedance
- $Z_{IN} = (50 \times 1.4)\Omega + (50 \times -j0.8)\Omega = 70 - j40\Omega$

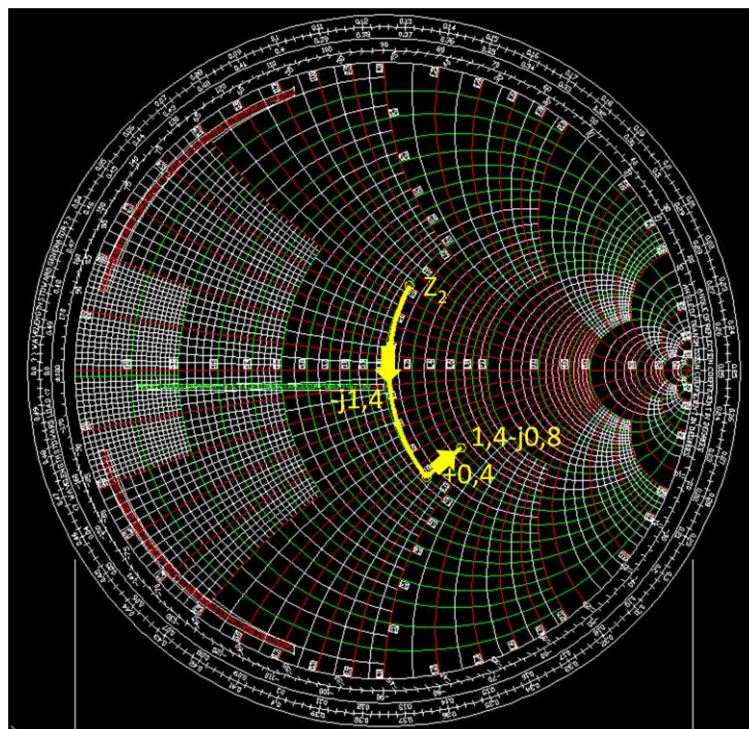

Kuva 1: Impedances in Series

2. Impedances in Parallel

Example: Find Z_{IN}

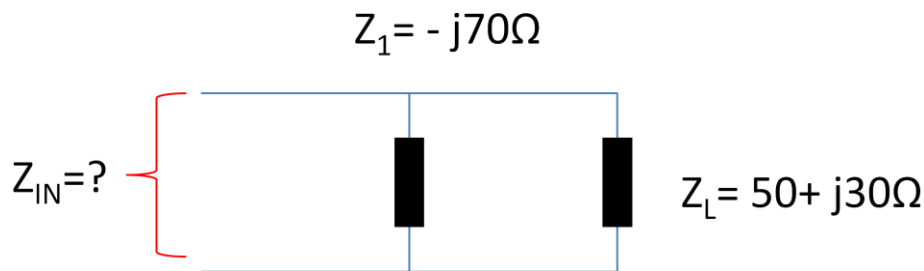


2.1 By calculation

$$\begin{aligned}
 Z_{IN} &= \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_L}} = \frac{1}{\frac{1}{-j70} + \frac{1}{50 + j30}} = \frac{1}{\frac{1}{70\angle -90^\circ} + \frac{1}{58,3\angle 30,96^\circ}} \\
 &= \frac{1}{0,0143\angle 90^\circ + 0,0172\angle -30,96^\circ} = \frac{1}{0 + j0,0143 + 0,0147 - j0,0088} \\
 &= \frac{1}{0,0147 + j0,0055} = \frac{1}{0,0157\angle 20,5^\circ} = 63,7\angle -20,5^\circ\Omega = \mathbf{59,7 - j22,3\Omega}
 \end{aligned}$$

2.2 Using Smith Chart

- Normalize ; $Z_L' = Z_L/50$, $Z_1' = Z_1/50$,
- $Z_L' = 1 + j0,6\Omega$ -> find point on the Smith chart.
- Find $1/Z_L' = Y_L'$ on the smith chart by "mirroring"
- $Z_1' = -j1,4\Omega$ -> Calculate $Y_1 = 1/1,4\angle 90 = 0 + j0,71S$
 - o On a constant conductance circle, from Y_1 rotate clockwise 0,71 units to arrive at Y_L
- Convert to $Z_L = 1,19 - j0,45$ by "mirroring"
- Convert back to system impedance
- $Z_{IN} = (50 \times 1,19)\Omega + (50 \times -j0,45)\Omega \approx \mathbf{59,7 - j22,3\Omega}$

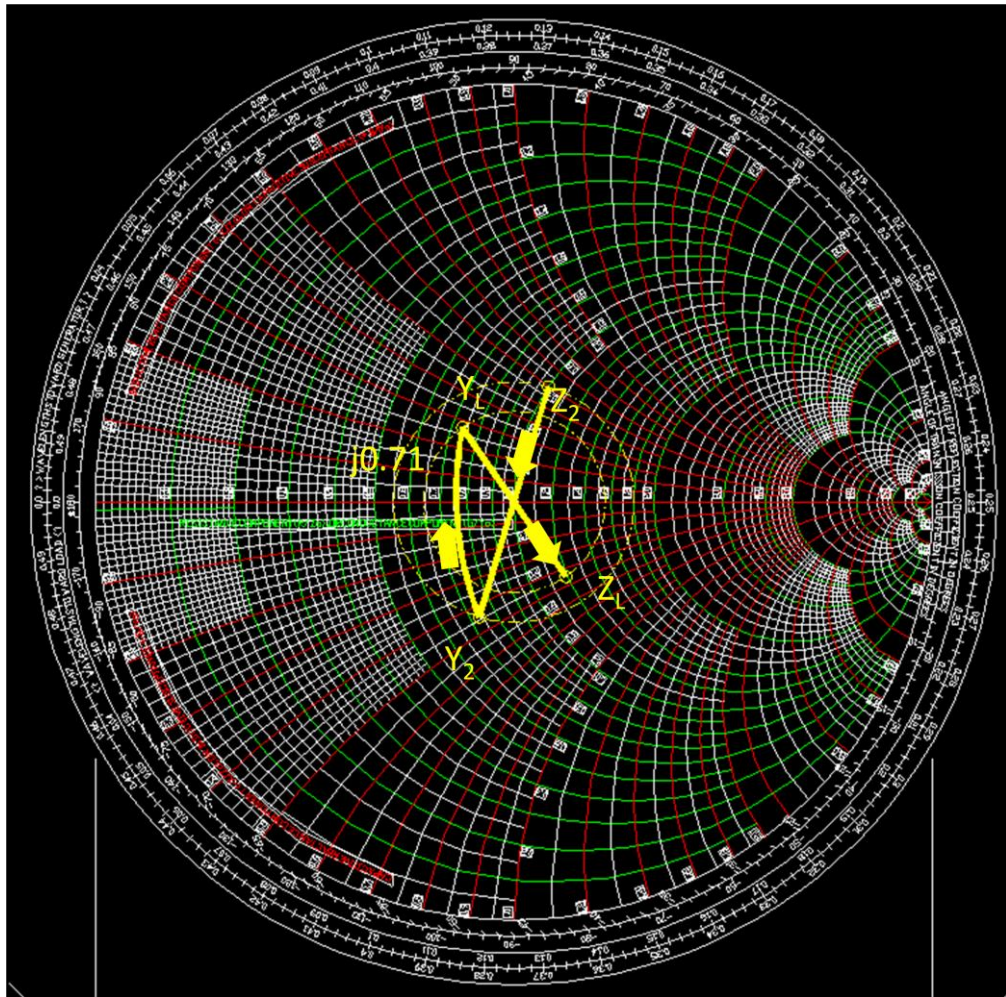


Kuva 2: Impedances in Parallel

3. Lossless transmission line, terminated with an arbitrary impedance

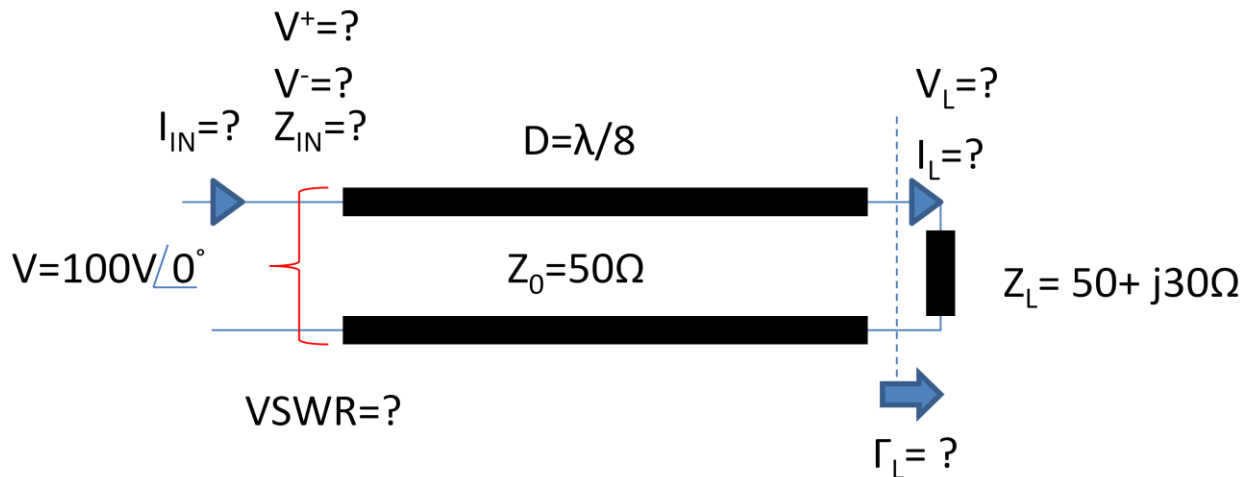3.1 Example:

Find Z_{IN} , I_{IN} , V_L , I_L , VSWR as a ratio and in dB, return loss in dB, complex voltage/current reflection coefficient and power reflection coefficient at load of the following circuit. Transmission line which length is $\lambda/8$ is assumed to be lossless. System impedance is 50Ω .



3.2 By calculation

Input impedance for a lossless transmission line terminated with a complex impedance is

$$Z_{IN} = Z_0 \frac{Z_L + jZ_0 \tan \beta D}{Z_0 + jZ_L \tan \beta D}$$

Kaava 1

where

Z_0 = system impedance;

Z_L = load impedance;

β = wave number = $2\pi/\lambda$;

λ = wavelength;

D = length of transmission line;

Wavelength is

$$\lambda = \frac{v_p}{f}$$

Where

v_p = Speed of propagation in the transmission line;

f = Frequency;

$$\begin{aligned} Z_{IN} &= 50 \frac{50 + j30 + j(50 \tan \frac{\pi}{4})}{50 + j(50 + j30)(\tan \frac{\pi}{4})} = 50 \frac{50 + j80}{50 + j50 - 30} = \frac{2500 + j4000}{20 + j50} = \frac{4716 \angle 58,0^\circ}{53,85 \angle 68,2^\circ} \\ &= 86,2 - j15,5 \, \Omega = \mathbf{87,6 \angle -10,2^\circ \, \Omega} \end{aligned}$$

and

$$I_{IN} = \frac{V_{IN}}{Z_{IN}} = \frac{100 \angle 0^\circ}{87,6 \angle -10,2^\circ} = \mathbf{1,14 \angle 10,2^\circ \, A}$$

Wave functions for voltage and current as function of distance z ($z=0$ at generator side of the line) in lossless transmission line are

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{Z_0} + e^{(-j\beta z)} - \frac{V^-}{Z_0} e^{(j\beta z)}$$

Where

V^+ = forward propagating voltage wave

V^- = backward propagating voltage wave

at $z=0$ voltage and current must be

$$V(0) = V^+ + V^- = 100V \angle 0^\circ$$

$$I(0) = I_{IN} = \frac{V^+}{Z_0} - \frac{V^-}{Z_0} = 1,14 \angle 10,2^\circ A$$

Solve $V(0)$ and $I(0)$ from above by substitution:

$$I(0) = \frac{100 \angle 0^\circ - V^-}{50} - \frac{V^-}{50} = 1,14 \angle 10,2^\circ \Rightarrow$$

$$V^- = \frac{100 \angle 0^\circ - 57 \angle 10,2^\circ}{2} = \mathbf{22,52 \angle -12,95^\circ V} = 21,95 - j5,05 V$$

$$V^+ = 100 \angle 0^\circ - 22,52 \angle -12,95^\circ = 78,05 + j5,05 = \mathbf{78,21 \angle +3,7^\circ V}$$

And check

$$V^+ + V^- = 78,05 + j5,05 + 21,95 - j5,05 = 100 \angle 0^\circ V; OK$$

Solve V_L and I_L at distance $D = \beta D = \pi/4$

$$V(D) = V^+ e^{(-j\pi/4)} + V^- e^{(j\pi/4)}$$

$$I(D) = \frac{V^+}{Z_0} e^{(-j\pi/4)} - \frac{V^-}{Z_0} e^{(j\pi/4)}$$

using Euler's formula

$$e^{j\varphi} = \cos\varphi + j\sin\varphi$$

$$V(D) = V^+ \left(\cos\left(\frac{-\pi}{4}\right) + j\sin\left(\frac{-\pi}{4}\right) \right) + V^- \left(\cos\left(\frac{\pi}{4}\right) + j\sin\left(\frac{\pi}{4}\right) \right)$$

$$I(D) = \frac{V^+}{Z_0} \left(\cos\left(\frac{-\pi}{4}\right) + j\sin\left(\frac{-\pi}{4}\right) \right) - \frac{V^-}{Z_0} \left(\cos\left(\frac{\pi}{4}\right) + j\sin\left(\frac{\pi}{4}\right) \right)$$

$$\mathbf{V(D)} = (78,05 + j5,05)(0,707 - j0,707) + (21,95 - j5,05)(0,707 + j0,707)$$

$$= 77,84 - j39,66 = \mathbf{87,36 \angle -27^\circ V}$$

$$\begin{aligned}
 I(D) &= \frac{78,05 + j5,05}{50} \left(\cos\left(\frac{-\pi}{4}\right) + j\sin\left(\frac{-\pi}{4}\right) \right) - \left(\frac{21,95 - j5,05}{50} \left(\cos\left(\frac{\pi}{4}\right) + j\sin\left(\frac{\pi}{4}\right) \right) \right) \\
 &= 1,556 + j0,1(0,7,7 - j0,707) - ((0,44 - j0,10)(0,707 + j0,707)) \\
 &= 0,79 - j1,27 = \mathbf{1,49 \angle -58,1^\circ A}
 \end{aligned}$$

Check that impedance at load is correct;

$$Z_L = \frac{V(D)}{I(D)} = \frac{87,36 \angle -27^\circ V}{1,49 \angle -58,1^\circ A} = 58,63 \angle 31,9^\circ \approx 50 + j30 \Omega$$

Voltage or current Reflection coefficient is (at load)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{50 + j30 - 50}{50 + j30 + 50} = \frac{30 \angle 90^\circ}{104,4 \angle 16,7^\circ} = \mathbf{0,287 \angle 73,3^\circ}$$

and at generator

$$\Gamma_G = \frac{Z_{IN} - Z_0}{Z_{IN} + Z_0}$$

$$\Gamma_G = \frac{86,2 - j15,5 - 50}{86,2 - j15,5 + 50} = \frac{39,4 \angle -23,1^\circ}{137,0 \angle -6,49^\circ} = \mathbf{0,287 \angle -16,6^\circ}$$

Return Loss in dB is

$$R = 20 \log |\Gamma|$$

$$\mathbf{R = 20 \log 0,287 = -10,7 \text{ dB}}$$

Power Reflection coefficient is

$$|s|^2 = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|^2$$

$$|s|^2 = \left| \frac{50 + j30 - 50}{50 + j30 + 50} \right|^2 = 0,297^2 = \mathbf{0,082}$$

Voltage Standing Wave Ratio is

$$\begin{aligned}
 VSWR &= \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \\
 \frac{VSWR}{dB} &= 20 \log \left(\frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \right)
 \end{aligned}$$

$$VSWR = \frac{1 + 0,287}{1 - 0,287} = \mathbf{1,82}$$


$$\mathbf{VSWR = 20 \log 1,82 = 5,2 \text{ dB}}$$

3.3 Using Smith Chart

Many of the above parameters can be read directly from the Smith Chart without calculation and others calculated by using them.


1. Normalize ; $Z_L' = Z_L/50$, $Z_L' = 1 + j0,6\Omega$ -> find point on the Smith chart
2. Draw a circle to that point with its center in the center of the chart
3. From center point extend a line through Z_L' to the scale "wavelengths towards generator" -> read " λ at load# = 0,148
4. Move on the scale towards generator (clockwise) and add transmission line's $\lambda/8 = 0,125$ units and arrive to " λ at generator" = 0,273
5. Draw a line from point λ at generator to the center of the Smith Chart, read $Z_{IN}' = 1,83 - j0,3$
6. Convert Z_{IN}' back to system impedance level 50Ω

$$Z_{IN} = 50 \times 1,74 - 50 \times j0,3 \approx 87 - j15\Omega$$

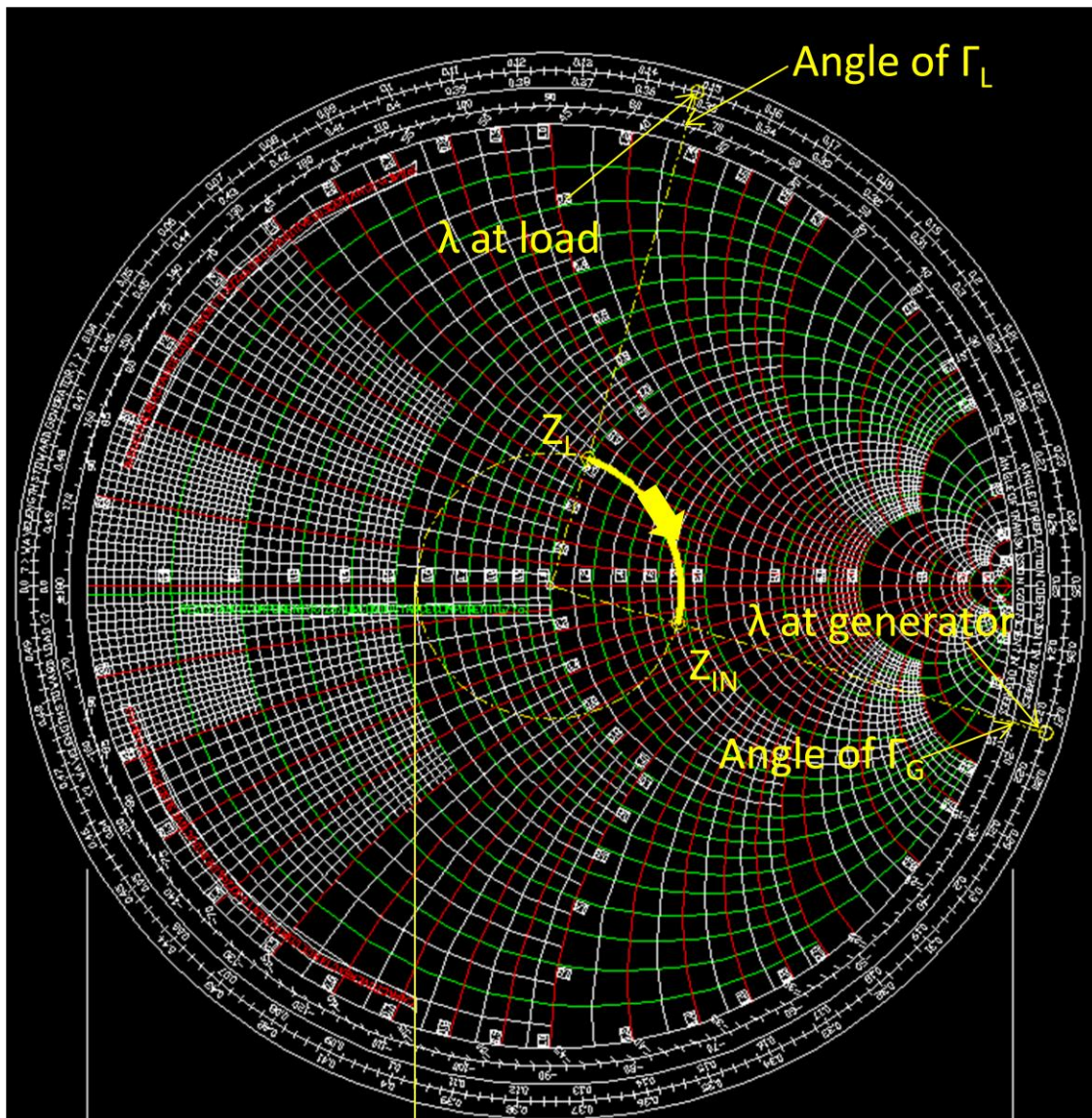

Kuva 3: Transmission line

- From the circle drawn above, draw from the crossing of the circle and the horizontal axis a straight line down to “radially scaled parameters”

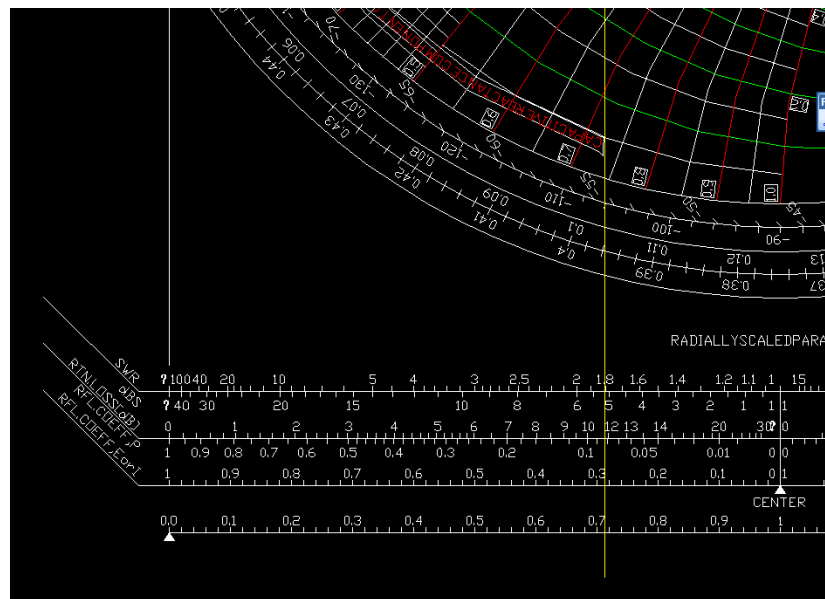

Kuva 4:Radially scaled parameters, SWR, Return Loss, Reflection Coefficient


- From the scale “SWR” read SWR $\approx 1,82$
- From the scale “dBs” read SWR in dB $\approx 5,2$ dB
- From the scale “RTN LOSS(dB)” read R in dB $\approx -10,7$ dB
- From the scale “RFL COEFF,P” read power reflection coefficient $|s|^2 \approx 0,082$
- From the scale “RFL COEFF,E or I” read reflection coefficient for voltage or current $|\Gamma_L| = |\Gamma_G| \approx 0,285$
- From the circular scale “Angle of reflection coefficient” read in the intersection of lines drawn in steps 3 and 5 and this scale the corresponding angles of reflection coefficient , angle of $\Gamma_L \approx 73^\circ$ and angle of $\Gamma_G \approx 16,6^\circ$

4. Distance to first voltage maximum and minimum

5. Impedance matching

5.1 Shunt-series L-Network, by calculation

Load impedance $Z_0 = R_L + jX_L$ shall be matched to system impedance Z_0 to maximize power transfer from generator to load. Matching L- network consists of shunt susceptance jB and series reactance jX .

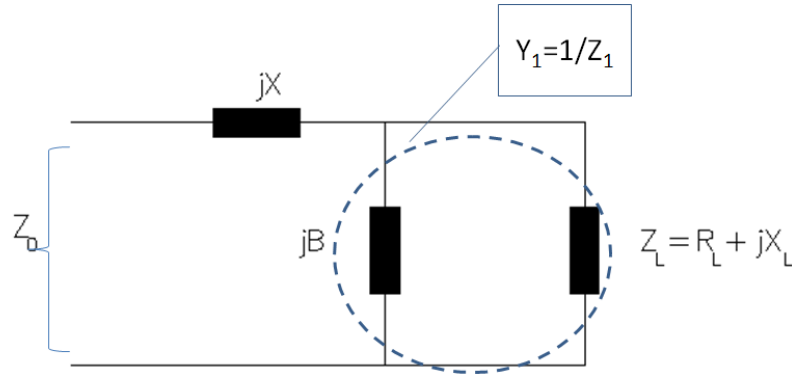

Kuva 5:L-network matching

Calculate first impedance Z_1 , Load Z_L in parallel with jB

$$Z_1 = \frac{\frac{1}{jB}(R_L + jX_L)}{\frac{1}{jB} + (R_L + jX_L)} = \frac{(R_L + jX_L)}{1 - BX_L + jR_L B}$$

Develop Z_1 further to separate its **real** and **imaginary** parts:

- Multiply numerator and denominator of Z_1 with $(1 - BX_L - jR_L B) \rightarrow$

$$\begin{aligned} Z_1 &= \frac{(R_L + jX_L)(1 - BX_L - jR_L B)}{(1 - X_L B)^2 + R_L^2 B^2} = \frac{R_L - \cancel{R_L B X_L} + \cancel{R_L B X_L} + j(X_L - BX_L^2 - R_L^2 B)}{(1 - X_L B)^2 + R_L^2 B^2} \\ &= \frac{R_L + j(X_L - BX_L^2 - R_L^2 B)}{1 + X_L^2 B^2 - 2X_L B + R_L^2 B^2} = \frac{\textcolor{green}{R_L} + j(\textcolor{red}{X_L - BX_L^2 - R_L^2 B})}{(\textcolor{blue}{R_L^2 + X_L^2})B^2 - 2X_L B + 1} \end{aligned}$$

Real part of Z_1 has to be equal to the system impedance $Z_0 \rightarrow$ Solve B to fulfill that condition

$$\frac{\textcolor{green}{R_L}}{(\textcolor{blue}{R_L^2 + X_L^2})B^2 - 2X_L B + 1} = Z_0$$

$$\begin{aligned} (R_L^2 + X_L^2)B^2 - 2X_L B + 1 &= \frac{R_L}{Z_0} \rightarrow \\ Z_0(R_L^2 + X_L^2)B^2 - 2Z_0 X_L B + (Z_0 - R_L) &= 0 \end{aligned}$$

This is a quadratic equation which roots are

$$\begin{aligned} B &= \frac{2Z_0 X_L \pm \sqrt{(2Z_0 X_L)^2 - 4Z_0(R_L^2 + X_L^2)(Z_0 - R_L)}}{2Z_0(R_L^2 + X_L^2)} \\ &= \frac{Z_0 X_L \pm \sqrt{Z_0^2 X_L^2 - (R_L^2 + X_L^2)(Z_0^2 - Z_0 R_L)}}{Z_0(R_L^2 + X_L^2)} \\ &= \frac{Z_0 X_L \pm \sqrt{Z_0^2 X_L^2 - R_L^2 Z_0^2 + R_L^3 Z_0 - Z_0^2 X_L^2 + X_L^2 R_L Z_0}}{Z_0(R_L^2 + X_L^2)} \end{aligned}$$

$$\begin{aligned}
&= \frac{Z_0 X_L \pm \sqrt{Z_0(X_L^2 Z_0) - Z_0(R_L^2 Z_0) + Z_0 R_L^3 - Z_0(X_L^2 Z_0) + Z_0(X_L^2 R_L)}}{Z_0(R_L^2 + X_L^2)} \\
&= \frac{Z_0 X_L \pm \sqrt{Z_0(\cancel{X_L^2 Z_0} - R_L^2 Z_0 + R_L^3 - \cancel{X_L^2 Z_0} + X_L^2 R_L)}}{Z_0(R_L^2 + X_L^2)} \\
&= \frac{Z_0 X_L \pm \sqrt{Z_0(-R_L^2 Z_0 + R_L^3 + X_L^2 R_L)}}{Z_0(R_L^2 + X_L^2)} \\
&= \frac{\frac{Z_0 X_L}{Z_0} \pm \sqrt{\left(\frac{1}{Z_0}\right)^2 Z_0(-R_L^2 Z_0 + R_L^3 + X_L^2 R_L)}}{\frac{Z_0(R_L^2 + X_L^2)}{Z_0}} \\
&= \frac{X_L \pm \sqrt{\frac{1}{Z_0} R_L(R_L^2 + X_L^2 - R_L Z_0)}}{(R_L^2 + X_L^2)} \rightarrow \\
&\boxed{B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0}} \sqrt{(R_L^2 + X_L^2 - R_L Z_0)}}{(R_L^2 + X_L^2)}}
\end{aligned}$$

Kaava 2

Series reactance jX has to compensate the imaginary part of Z_1

$$\frac{(X_L - BX_L^2 - R_L^2 B)}{(R_L^2 + X_L^2)B^2 - 2X_L B + 1} = -X$$

and because

$$\frac{R_L}{(R_L^2 + X_L^2)B^2 - 2X_L B + 1} = \frac{R_L}{\frac{R_L}{Z_0}} = Z_0$$


$$\frac{(X_L - BX_L^2 - R_L^2 B)}{\frac{R_L}{Z_0}} = -X$$

$$-X = \frac{X_L - (X_L^2 + R_L^2)B}{\frac{R_L}{Z_0}} = \frac{-Z_0 X_L + B Z_0 (X_L^2 + R_L^2)}{R_L} \rightarrow$$


$$\boxed{X = \frac{B Z_0 (R_L^2 + X_L^2) - Z_0 X_L}{R_L}}$$

Kaava 3

5.1.1 Example: Match load

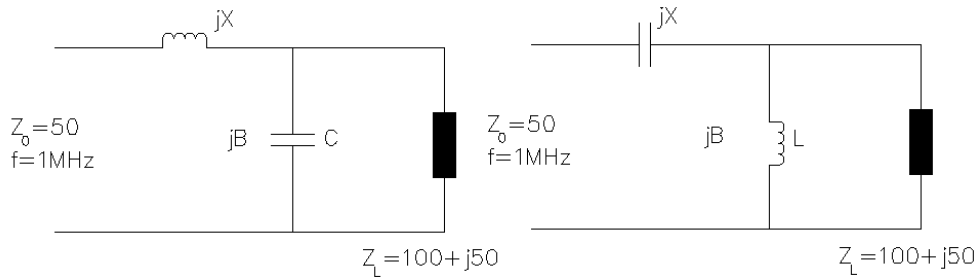


Shunt C, series L	Shunt L, series C
$B = \frac{X_L + \sqrt{\frac{R_L}{Z_0}} \sqrt{(R_L^2 + X_L^2 - R_L Z_0)}}{(R_L^2 + X_L^2)}$ $= \frac{50 + \sqrt{\frac{100}{50}} \sqrt{100^2 + 50^2 - 100 * 50}}{100^2 + 50^2}$ $= 0,013798S = 72,47\Omega \text{ (capacitor)}$	$B = \frac{X_L - \sqrt{\frac{R_L}{Z_0}} \sqrt{(R_L^2 + X_L^2 - R_L Z_0)}}{(R_L^2 + X_L^2)}$ $= \frac{50 - \sqrt{\frac{100}{50}} \sqrt{100^2 + 50^2 - 100 * 50}}{100^2 + 50^2}$ $= -0,005798S = -172,47\Omega \text{ (inductor)}$
$Y_L = \frac{1}{100 + j50} = 0,008 - j0,004S$	$Y_L = \frac{1}{100 + j50} = 0,008 - j0,004S$
$Y_1 = 0,008 - j0,004 + j0,013798$ $= 0,008 + j0,009798S$	$Y_1 = 0,008 - j0,004 - j0,005798$ $= 0,008 - j0,009798S$
$Z_1 = \frac{1}{Y_1} = \frac{1}{0,008 + j0,009798} = 50,00 - 61,23\Omega$	$Z_1 = \frac{1}{Y_1} = \frac{1}{0,008 - j0,009798} = 50,00 + 61,23\Omega$
$C = \frac{1}{72,47 * 2\pi * 1 * 10^6} F = 2,197nF$	$L = \frac{172,47}{2\pi * 1 * 10^6} H = 27,4uH$
$X = \frac{BZ_0(R_L^2 + X_L^2) - Z_0X_L}{R_L}$ $= \frac{0,013798 * 50(100^2 + 50^2) - 50 * 50}{100}$ $= 61,23\Omega \text{ (inductor)}$	$X = \frac{BZ_0(R_L^2 + X_L^2) - Z_0X_L}{R_L}$ $= \frac{-0,005798S * 50(100^2 + 50^2) - 50 * 50}{100}$ $= -61,23\Omega \text{ (capacitor)}$
$L = \frac{61,23}{2\pi * 1 * 10^6} H = 9,75uH$	$C = \frac{1}{61,23 * 2\pi * 1 * 10^6} F = 2,600nF$

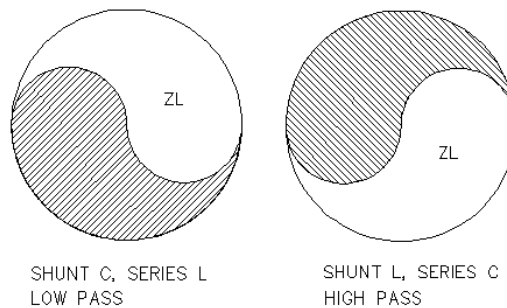

Kuva 6: Allowable Load impedance area for shunt-series network in Smith Chart representation

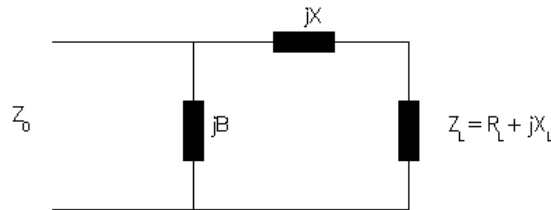5.2 Series shunt- L-Network, by calculation

Matching L- network consists of a series reactance jX and a shunt susceptance jB .



Calculate first impedance Z_1 , Load Z_L in series with jX

$$Z_1 = jX + R_L + jX_L = j(X_L + X)$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_L + j(X_L + X)}$$

Develop Y_1 to separate its real and imaginary parts, multiply numerator and denominator by $R_L - j(X_L + X)$

$$Y_1 = \frac{R_L - j(X_L + X)}{R_L^2 - (j(X_L + X))^2} = \frac{R_L - j(X_L + X)}{R_L^2 + X_L^2 + X^2 + 2X_LX}$$

Real part of admittance Y_1 must be equal to $1/Z_0 \rightarrow$

$$\frac{R_L}{R_L^2 + X_L^2 + X^2 + 2X_LX} = \frac{1}{Z_0} \rightarrow$$

$$X^2 + 2X_LX + R_L^2 + X_L^2 - R_LZ_0 = 0 \rightarrow$$

$$X = \frac{-2X_L \pm \sqrt{(2X_L)^2 - 4(R_L^2 + X_L^2 - R_LZ_0)}}{2} \rightarrow$$

$$\boxed{X = -X_L \pm \sqrt{R_L(Z_0 - R_L)}}$$

Kaava 4

Imaginary part of admittance Y_1 has to be compensated by B , and


$$\frac{X_L + X}{R_LZ_0} = \frac{\cancel{X_L} - \cancel{X_L} \pm \sqrt{R_L(Z_0 - R_L)}}{R_LZ_0} = \frac{\frac{1}{R_L} \pm \sqrt{R_L(Z_0 - R_L)}}{\frac{1}{R_L} R_LZ_0} = -B \rightarrow$$

$$\boxed{B = \frac{\pm \sqrt{\frac{(Z_0 - R_L)}{R_L}}}{Z_0}}$$


Kaava 5

5.2.1 Example: Match load


L-network match, series- shunt

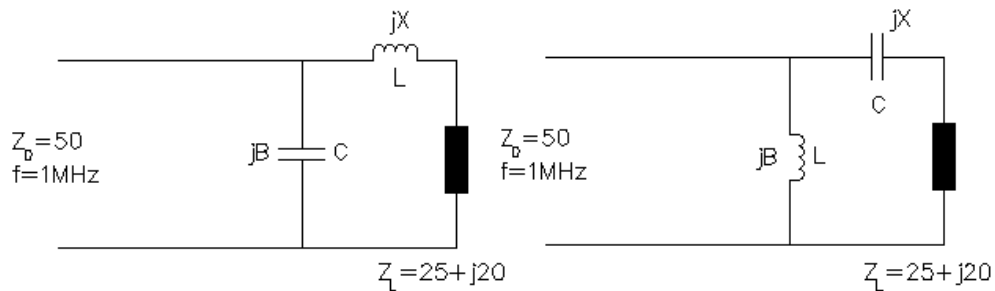

Series L, Shunt C	Series C, Shunt L
$X = -X_L + \sqrt{R_L(Z_0 - R_L)}$ $= -(20) + \sqrt{25(50 - 25)}$ $= 5,00\Omega$	$X = -X_L - \sqrt{R_L(Z_0 - R_L)}$ $= -(20) - \sqrt{25(50 - 25)}$ $= -45,00\Omega$
$B = \frac{+\sqrt{\frac{(Z_0 - R_L)}{R_L}}}{Z_0} = \frac{+\sqrt{\frac{(50 - 25)}{25}}}{50} = 0,020S$	$B = \frac{-\sqrt{\frac{(Z_0 - R_L)}{R_L}}}{Z_0} = \frac{-\sqrt{\frac{(50 - 25)}{25}}}{50} = -0,020S$
$C = \frac{0,020}{2\pi * 1 * 10^6} = 3,18nF$	$L = \frac{1/0,020}{2\pi * 1 * 10^6} = 7,96uH$
$L = \frac{5,00}{2\pi * 1 * 10^6} = 796nH$	$C = \frac{1}{45,00 * 2\pi * 1 * 10^6} = 3,53nF$

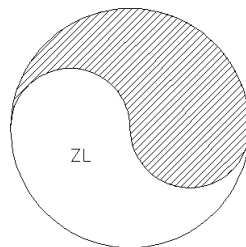


SERIES L, SHUNT C

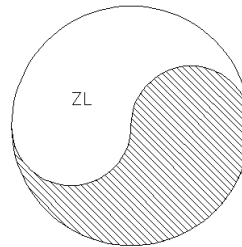


SERIES C, SHUNT L

Kuva 7: Allowable Load impedance area for series -shunt -network in Smith Chart representation


5.2.2 Example: Match load

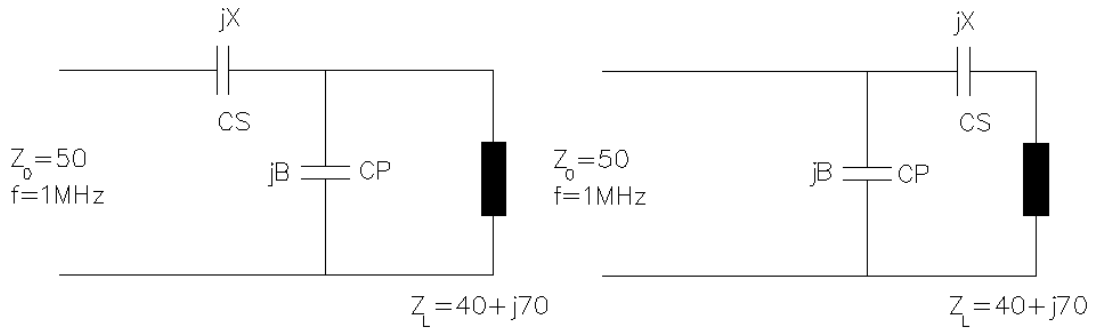

Shunt C, series C	Series C, shunt C
$B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0}} \sqrt{(R_L^2 + X_L^2 - R_L Z_0)}}{(R_L^2 + X_L^2)}$ $= \frac{70 \pm \sqrt{\frac{40}{50}} \sqrt{(40^2 + 70^2 - 40 * 50)}}{(40^2 + 70^2)}$ $= 0,020S \text{ (not applicable, would require L in series)}$ $= 0,001538S$	$X = -X_L \pm \sqrt{R_L(Z_0 - R_L)}$ $= -70 \pm \sqrt{40(50 - 40)}$ $= -50,00\Omega$ $= -90,00\Omega \text{ (not applicable, would require L in parallel)}$
$CP = \frac{0,001531}{2\pi * 1 * 10^6} F = 244,9pF$	$CS = \frac{1}{50,00 * 2\pi * 1 * 10^6} F = 3,18nF$
$X = \frac{BZ_0(R_L^2 + X_L^2) - Z_0 X_L}{R_L}$ $= \frac{0,001538 * 50(40^2 + 70^2) - 50 * 70}{40}$ $= -75,00\Omega \text{ (capacitor)}$	$B = \frac{\pm \sqrt{\frac{(Z_0 - R_L)}{R_L}}}{Z_0} = \pm \sqrt{\frac{(50 - 40)}{40}}$ $= 0,010S \text{ (capacitor)}$ $= -0,010S \text{ (inductor, not applicable)}$
$CS = \frac{1}{75,00 * 2\pi * 1 * 10^6} F = 2,12nF$	$CP = \frac{0,010}{2\pi * 1 * 10^6} F = 1,59nF$

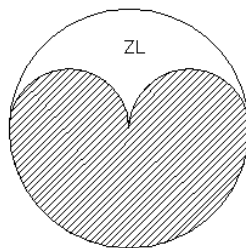


SHUNT C, SERIES C

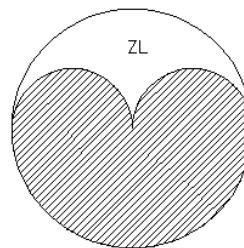


SERIES C, SHUNT C

Kuva 8 Allowable Load impedance area for capacitors only-network in Smith Chart representation

5.2.3 Example: Match load

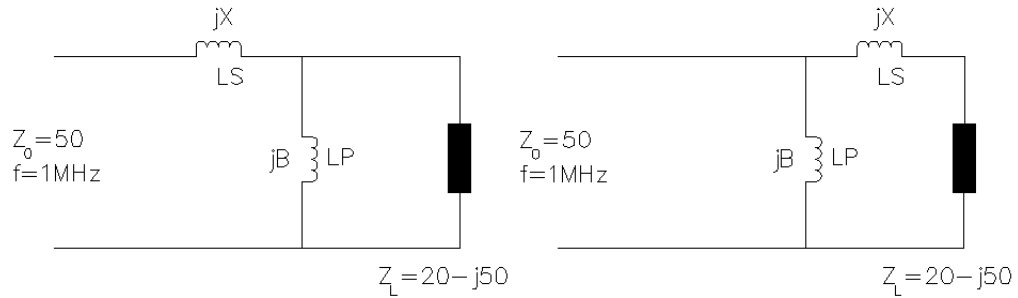


Shunt L, series L	Series L, shunt L
$B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0} \sqrt{(R_L^2 + X_L^2 - R_L Z_0)}}}{(R_L^2 + X_L^2)}$ $= \frac{-50 \pm \sqrt{\frac{20}{50} \sqrt{(20^2 + (-50)^2 - 20 * 50)}}}{(20^2 + (-50)^2)}$ $= -0,00773S$ $= -0,02674S \text{ (not applicable, would require series C)}$	$X = -X_L \pm \sqrt{R_L(Z_0 - R_L)}$ $= -(-50) \pm \sqrt{20(50 - 20)}$ $= 74,49\Omega \text{ (not applicable, would require shunt C)}$ $= 25,51\Omega$
$LP = \frac{1}{0,00773 * 2\pi * 1 * 10^6} H = 20,6\mu H$	$LS = \frac{25,51}{2\pi * 1 * 10^6} H = 4,06\mu H$
$X = \frac{BZ_0(R_L^2 + X_L^2) - Z_0X_L}{R_L}$ $= \frac{-0,00773 * 50(20^2 + (-50)^2) - 50 * (-50)}{20}$ $= 68,96\Omega$	$B = \frac{\pm \sqrt{\frac{(Z_0 - R_L)}{R_L}}}{Z_0} = \frac{\pm \sqrt{\frac{(50 - 20)}{20}}}{50}$ $= 0,0245S \text{ (capacitor, not applicable)}$ $= -0,0245S \text{ (inductor)}$
$LS = \frac{68,96}{2\pi * 1 * 10^6} H = 10,98\mu H$	$LP = \frac{1}{0,0245 * 2\pi * 1 * 10^6} H = 6,50\mu H$

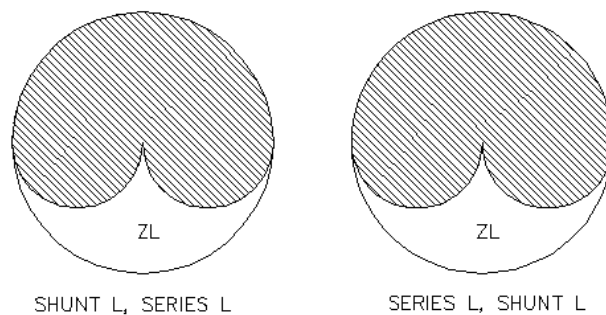

Kuva 9 Allowable Load impedance area for inductors only-network in Smith Chart representation

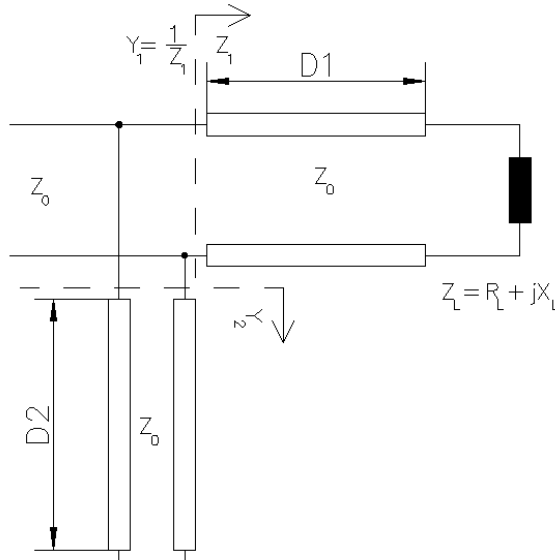5.3 Shorted parallel stub as tuning element

Load matching can be achieved by paralleling a length of a short circuited transmission line 2 (length D2) placed at a proper distance (transmission line length D1) from the load. Both transmission lines here are assumed to be lossless and having a characteristic impedance Z_0 .



Impedance towards the load as seen in front of transmission line 1 is

$$Z_1 = Z_0 \frac{Z_L + jZ_0 \tan \beta D1}{Z_0 + jZ_L \tan \beta D1} = \frac{Z_0 [(R_L + jX_L) + jZ_0 \tan \beta D1]}{Z_0 + j[(R_L + jX_L) \tan \beta D1]} = \frac{Z_0 R_L + jZ_0 X_L + jZ_0^2 \tan \beta D1}{Z_0 - X_L \tan \beta D1 + jR_L \tan \beta D1}$$

$$Y_1 = \frac{Z_0 - X_L \tan \beta D1 + jR_L \tan \beta D1}{Z_0 R_L + jZ_0 X_L + jZ_0^2 \tan \beta D1} = \frac{Z_0 - X_L \tan \beta D1 + jR_L \tan \beta D1}{Z_0 R_L + j(Z_0 X_L + Z_0^2 \tan \beta D1)}$$

Develop Y_1 further to separate its **real** and **imaginary** parts: multiply numerator and denominator by $(Z_0 R_L - j(Z_0 X_L + Z_0^2 \tan \beta D1))$

$$Y_1 = \frac{(Z_0 - X_L \tan \beta D1 + jR_L \tan \beta D1)(Z_0 R_L - jZ_0 X_L - jZ_0^2 \tan \beta D1)}{Z_0^2 R_L^2 + Z_0^2 X_L^2 + 2Z_0^3 X_L \tan \beta D1 + Z_0^4 \tan^2 \beta D1}$$

$$= \frac{\begin{aligned} &Z_0^2 R_L - jZ_0^2 X_L - jZ_0^3 \tan \beta D1 - Z_0 R_L X_L \tan \beta D1 + jZ_0 X_L^2 \tan \beta D1 + jZ_0^2 X_L \tan^2 \beta D1 \\ &+ jZ_0 R_L^2 \tan \beta D1 + Z_0 R_L X_L \tan \beta D1 + Z_0^2 R_L \tan^2 \beta D1 \end{aligned}}{Z_0^2 (R_L^2 + X_L^2 + 2Z_0 X_L \tan \beta D1 + Z_0^2 \tan^2 \beta D1)}$$

$$Y_1 = \frac{Z_0^2 R_L (1 + \tan^2 \beta D1) + jZ_0^2 (-X_L - Z_0 \tan \beta D1 + \frac{X_L^2}{Z_0} \tan \beta D1 + X_L \tan^2 \beta D1 + \frac{R_L^2}{Z_0} \tan \beta D1)}{Z_0^2 (R_L^2 + X_L^2 + 2Z_0 X_L \tan \beta D1 + Z_0^2 \tan^2 \beta D1)}$$

real part of admittance Y_1 has to be equal to $1/Z_0$, because stub to be calculated later will compensate the imaginary part->

$$\frac{R_L(1 + \tan^2 \beta D1)}{R_L^2 + X_L^2 + 2Z_0 X_L \tan \beta D1 + Z_0^2 \tan^2 \beta D1} = \frac{1}{Z_0} \rightarrow$$

$$Z_0^2 \tan^2 \beta D1 R_L^2 - R_L Z_0 \tan^2 \beta D1 + 2Z_0 X_L \tan \beta D1 + X_L^2 - R_L Z_0 = 0 \rightarrow$$

$$(Z_0^2 - R_L Z_0) \tan^2 \beta D1 + 2Z_0 X_L \tan \beta D1 + R_L^2 + X_L^2 - R_L Z_0 = 0 \rightarrow$$

$$\beta D1 = \text{atan} \left(\frac{-2Z_0 X_L \pm \sqrt{(2Z_0 X_L)^2 - 4(Z_0^2 - R_L Z_0)(R_L^2 + X_L^2 - R_L Z_0)}}{2(Z_0^2 - R_L Z_0)} \right)$$

Kaava 6: Length of transmission line in shorted stub matching

Only the positive root is meaningful.

Length of transmission line D1 is

$$D1 = \frac{\beta D1}{2\pi} \lambda$$

Impedance Z_2 of the shorted stub of length D2 is, because $Z_{L, \text{stub}} = 0$

$$Z_2 = Z_0 \frac{jZ_0 \tan \beta D1}{Z_0} = jZ_0 \tan \beta D1 \rightarrow Y_2 = \frac{1}{jZ_0 \tan \beta D2},$$

therefore

$$\frac{j(-X_L - Z_0 \tan \beta D1 + \frac{X_L^2}{Z_0} \tan \beta D1 + X_L \tan^2 \beta D1 + \frac{R_L^2}{Z_0} \tan \beta D1)}{R_L(1 + \tan^2 \beta D1)Z_0} = \frac{1}{-jZ_0 \tan \beta D2} \rightarrow$$

$$\beta D2 = \text{atan} \left(\frac{R_L(1 + \tan^2 \beta D1)}{\tan \beta D1 \left(-Z_0 + \frac{X_L^2}{Z_0} + X_L \tan \beta D1 + \frac{R_L^2}{Z_0} \right) - X_L} \right)$$


Kaava 7: Length of shorted stub in shorted stub matching

Length of stub D2 is

$$D2 = \frac{\beta D2}{2\pi} \lambda$$

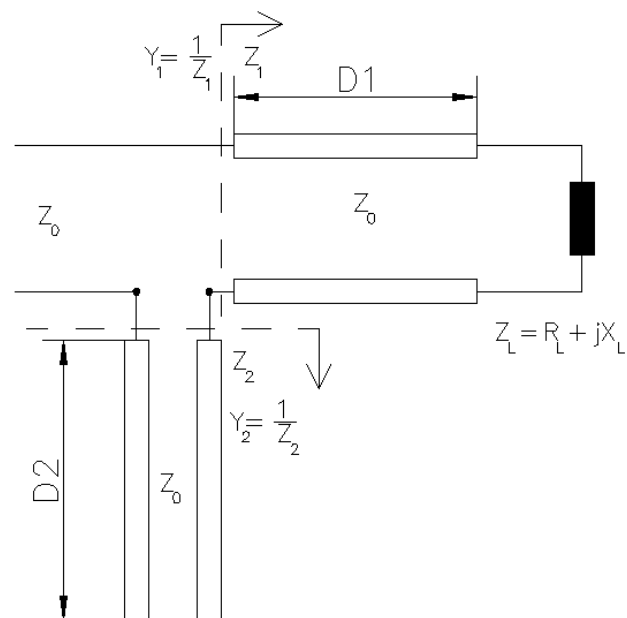5.4 Open series stub as tuning element

Load matching can be achieved by a length of a open transmission line 2 (length D2) placed in series at a proper distance (transmission line length D1) from the load. Both transmission lines here are assumed to be lossless and having a characteristic impedance Z_0 .



6. Lossy transmission line terminated with an arbitrary impedance

Wave functions for voltage and current as function of distance z ($z=0$ at generator side of the line) for a lossy transmission line are

$$V(z) = V^+ e^{(-\gamma z)} + V^- e^{(\gamma z)}$$

$$I(z) = \frac{V^+}{Z_0} e^{(-\gamma z)} - \frac{V^-}{Z_0} e^{(\gamma z)}$$

Where

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Kaava 8: Propagation constant

γ = Propagation constant $[\gamma] = \frac{1}{m}$

α = Attenuation constant $[\alpha] = \frac{1}{m}$; $\alpha/\text{dB} = 20 \log e^\alpha = 20\alpha \log e = 8,686 \alpha$


β = Phase constant $[\beta] = \frac{\text{rad}}{m}$

R, L, G, C = Transmission line distributed constants

The velocity of propagation or the phase velocity is given by

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$


Kaava 9: Speed of propagation

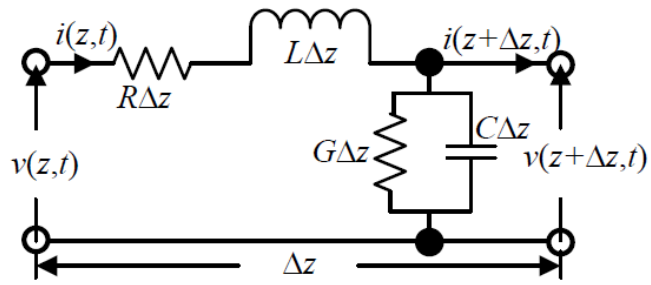

and the characteristic impedance Z_0 is

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

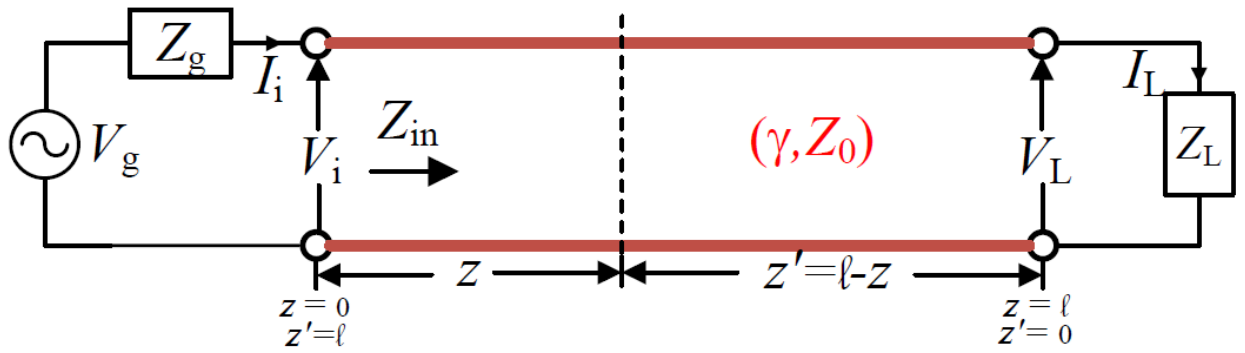Kaava 10: Characteristic impedance of a lossy transmission line



$$Z_L = \frac{V_L}{I_L} = \frac{V^+ e^{(-\gamma l)} + V^- e^{(\gamma l)}}{\frac{V^+}{Z_0} e^{(-\gamma l)} - \frac{V^-}{Z_0} e^{(\gamma l)}}$$

Because

$$V_L = V(l) = V^+ e^{(-\gamma l)} + V^- e^{(\gamma l)} \rightarrow V^+ e^{(-\gamma l)} = V_L - V^- e^{(\gamma l)}$$

$$I_L = I(l) = \frac{V^+}{Z_0} e^{(-\gamma l)} - \frac{V^-}{Z_0} e^{(\gamma l)}$$

V^- and V^+ can be solved

$$I_L = \frac{V_L - V^- e^{(\gamma l)}}{Z_0} - \frac{V^- e^{(\gamma l)}}{Z_0}$$

$$\rightarrow V^- = \frac{1}{2} (V_L - I_L Z_0) e^{(-\gamma l)} = \frac{I_L}{2} (Z_L - Z_0) e^{(-\gamma l)}$$

$$V_L = V^+ e^{(-\gamma l)} + V^- e^{(\gamma l)} = V^+ e^{(-\gamma l)} + \frac{1}{2} (V_L - I_L Z_0) e^{(-\gamma l)} e^{(-\gamma l)}$$

$$\rightarrow V^+ = \frac{1}{2}(V_L + I_L Z_0)e^{(\gamma l)} = \frac{I_L}{2}(Z_L + Z_0)e^{(\gamma l)}$$

and $V(z)$ and $I(z)$ now expressed as

$$V(z) = V^+e^{(-\gamma z)} + V^-e^{(\gamma z)}$$

$$V(z) = \frac{I_L}{2}[(Z_L + Z_0)e^{\gamma(l-z)} + (Z_L - Z_0)e^{-\gamma(l-z)}]$$

$$I(z) = \frac{V^+}{Z_0}e^{(-\gamma z)} - \frac{V^-}{Z_0}e^{(\gamma z)}$$

$$I(z) = \frac{I_L}{2Z_0}[(Z_L + Z_0)e^{\gamma(l-z)} - (Z_L - Z_0)e^{-\gamma(l-z)}]$$

and by assigning $z' = l-z$;

$$V(z) = \frac{I_L}{2}[(Z_L + Z_0)e^{\gamma z'} + (Z_L - Z_0)e^{-\gamma z'}]$$

$$I(z) = \frac{I_L}{2Z_0}[(Z_L + Z_0)e^{\gamma z'} - (Z_L - Z_0)e^{-\gamma z'}]$$

These functions can be written as

$$V(z') = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma z'} + \frac{I_L}{2}(Z_L - Z_0)e^{-\gamma z'} = \frac{I_L Z_L e^{\gamma z'} + I_L Z_0 e^{\gamma z'}}{2} + \frac{I_L Z_L e^{-\gamma z'} - I_L Z_0 e^{-\gamma z'}}{2}$$

$$= \frac{I_L Z_L e^{\gamma z'}}{2} + \frac{I_L Z_L e^{-\gamma z'}}{2} + \frac{I_L Z_0 e^{\gamma z'}}{2} - \frac{I_L Z_0 e^{-\gamma z'}}{2}$$

$$V(z') = I_L Z_L \left(\frac{e^{\gamma z'} + e^{-\gamma z'}}{2} \right) + I_L Z_0 \left(\frac{e^{\gamma z'} - e^{-\gamma z'}}{2} \right)$$

Because

$$\left(\frac{e^{\gamma z'} + e^{-\gamma z'}}{2} \right) = \cosh(\gamma z')$$

and

$$\left(\frac{e^{\gamma z'} - e^{-\gamma z'}}{2} \right) = \sinh(\gamma z')$$

$$\boxed{V(z') = I_L [Z_L \cosh(\gamma z') + Z_0 \sinh(\gamma z')]}$$

Kaava 11: Voltage of a lossy transmission line as function of distance

$$I(z) = \frac{I_L}{2Z_0}[(Z_L + Z_0)e^{\gamma z'} - (Z_L - Z_0)e^{-\gamma z'}] = \frac{I_L Z_L}{Z_0} \left(\frac{e^{\gamma z'} - e^{-\gamma z'}}{2} \right) + \frac{I_L Z_L}{Z_0} \left(\frac{e^{\gamma z'} + e^{-\gamma z'}}{2} \right)$$

$$\boxed{I(z') = \frac{I_L}{Z_0} [Z_L \sinh(\gamma z') + Z_0 \cosh(\gamma z')]}$$

Kaava 12: Current of a lossy transmission line as function of distance

Load impedance at distance z' from the load is

$$Z(z') = \frac{V_L}{I_L} = \frac{I_L [Z_L \cosh(\gamma z') + Z_0 \sinh(\gamma z')]}{\frac{I_L}{Z_0} [Z_L \sinh(\gamma z') + Z_0 \cosh(\gamma z')]} = Z_0 \frac{Z_L \cosh(\gamma z') + Z_0 \sinh(\gamma z')}{Z_L \sinh(\gamma z') + Z_0 \cosh(\gamma z')}$$

divide numerator and denominator by $\cosh(\gamma z')$ ->

$$Z(z') = Z_0 \frac{Z_L \frac{\cosh(\gamma z')}{\cosh(\gamma z')} + Z_0 \frac{\sinh(\gamma z')}{\cosh(\gamma z')}}{Z_L \frac{\sinh(\gamma z')}{\cosh(\gamma z')} + Z_0 \frac{\cosh(\gamma z')}{\cosh(\gamma z')}} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma z')}{Z_0 + Z_L \tanh(\gamma z')}$$

and when

$$\frac{\sinh(\gamma z')}{\cosh(\gamma z')} = \tanh(\gamma z')$$

$$Z(z') = Z_0 \frac{Z_L + Z_0 \tanh(\gamma z')}{Z_0 + Z_L \tanh(\gamma z')}$$

at generator, when $z' = l$

$$Z(z' = l) = Z_{IN} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$$

Kaava 13: Input impedance of a lossy transmission line

Furthermore, as $\gamma = \alpha + j\beta$ and

$$\tanh(x + jy) = \frac{\tanh(x) + j \tan(y)}{1 + j \tanh(x) \tan(y)}$$

$$Z_{IN} = Z_0 \frac{Z_L + Z_0 \left(\frac{\tanh(\alpha l) + j \tan(\beta l)}{1 + j \tanh(\alpha l) \tan(\beta l)} \right)}{Z_0 + Z_L \left(\frac{\tanh(\alpha l) + j \tan(\beta l)}{1 + j \tanh(\alpha l) \tan(\beta l)} \right)}$$

Power supplied by the generator is

$$P_{avG} = \frac{1}{2} \text{Re}[V_G I_{IN}^*]$$

Kaava 14: Power supplied by the generator

Power delivered to the load is

$$P_{avL} = \frac{1}{2} \text{Re}[V_L I_L^*] = \frac{1}{2} \left| \frac{V_L}{I_L} \right|^2 R_L = \frac{1}{2} |I_L|^2 R_L$$

Kaava 15: Power transmitted to load

Where

V_G, I_{IN}, V_L and I_L are the peak values of voltage and current.

Voltage reflection coefficient

$$\begin{cases} \Gamma(z) = \frac{V^- e^{\gamma z}}{V^+ e^{-\gamma z}} = \frac{V^-}{V^+} e^{2\gamma z} \\ V(z) = V^+ e^{(-\gamma z)} + V^- e^{(\gamma z)} \end{cases}$$

$$V(z) = V^+ e^{(-\gamma z)} [1 + \Gamma(z)]$$

$$I(z) = \frac{V^+}{Z_0} e^{(-\gamma z)} [1 + \Gamma(z)]$$

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

At load (z=l)

$$\Gamma(l) = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| e^{j\theta_\gamma}$$

Kaava 16: Voltage reflection coefficient at load

$$\Gamma(z) = \frac{V^-}{V^+} e^{2\gamma z} \rightarrow \frac{V^-}{V^+} = \Gamma(l) e^{-2\gamma l} = \Gamma_L e^{-2\gamma l}$$

At distance z


$$\Gamma(z) = \Gamma_L e^{-2\gamma l} e^{2\gamma z} = \Gamma_L e^{2\gamma(z-l)}$$

Voltage standing wave ratio is defined as

$$VSWR = \frac{|V_{max}|}{|V_{min}|} = S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Kaava 17: Voltage standing wave ratio

6.1 Example:

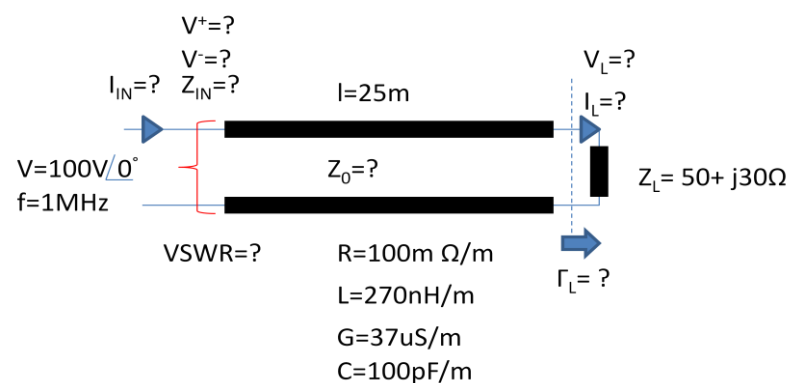

Calculate:

- Transmission line propagation constant γ
- Velocity of propagation in the transmission line
- Input impedance Z_{IN}
- Input current I_{IN}
- Characteristic impedance of transmission line Z_0
- Voltage at load V_L
- Load current I_L
- Transmission line voltage at 10m from the load
- Power delivered by the generator P_{avG}
- Power delivered to the load P_{avL}
- Voltage reflection coefficient at load Γ_L
- Voltage standing wave ratio VSWR

$$R = 100 \times 10^{-3} \Omega/m$$

$$L = 270 \times 10^{-9} H/m; j2\pi \times 10^6 \times 270 \times 10^{-9} = j1,696 \Omega/m$$

$$G = 37 \times 10^{-6} S/m$$

$$C = 100 \times 10^{-12} F/m; j2\pi \times 10^6 \times 100 \times 10^{-12} = j0,00063 S/m$$

Calculate γ , α and β from the distributed constants

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(100 \times 10^{-3} + j1,696)(37 \times 10^{-6} + j0,00063)} = \sqrt{-0,00106 + j0,000126}$$

$$= \sqrt{0,001072 \angle 173,26^\circ}$$

$$= \sqrt{0,001107 e^{j3,02387}} = (0,001107 e^{j3,02387})^{\frac{1}{2}} = 0,0332 e^{j1,5119} = 0,033 \angle 86,67^\circ$$

$$= \mathbf{0,00192 + j0,0331}$$

(other root 's real part is negative, meaningless here)

$$\alpha = \mathbf{0,00192 \frac{1}{m}}; \beta = \mathbf{0,033 \frac{rad}{m}}$$

Velocity of propagation is

$$u_p = \frac{\omega}{\beta} \approx \frac{1}{\sqrt{LC}} = \frac{2\pi \times 10^6}{0,033} = 190,5 * \frac{10^6 m}{s} \approx 0,635 c \text{ (63,5\% speed of light)}$$

Calculate Z_0 (Select root with positive real part)

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{(100 \times 10^{-3} + j1,696)}{(37 \times 10^{-6} + j0,00063)}} = \sqrt{2692,1 - j0,6227}$$

$$= \sqrt{2692,1 \angle -0,013252^\circ} = \sqrt{2692,1 e^{-j0,000231}} = 51,88 e^{-j0,0001156} = 51,89 \angle -0,00662^\circ$$

$$= \mathbf{51,88 - j0,0060 \Omega}$$

Calculate Z_{IN}

$$Z_{IN} = Z_0 \frac{Z_L + Z_0 \left(\frac{\tanh(\alpha l) + j \tanh(\beta l)}{1 + j \tanh(\alpha l) \tanh(\beta l)} \right)}{Z_0 + Z_L \left(\frac{\tanh(\alpha l) + j \tanh(\beta l)}{1 + j \tanh(\alpha l) \tanh(\beta l)} \right)}$$

$$\begin{aligned}
&= (51,8 - j0,0060) \frac{50 + j30 + (51,8 - j0,0060) \left(\frac{\tanh(0,00192x25) + j \tanh(0,033x25)}{1 + j \tanh(0,00192x25) \tanh(0,033x25)} \right)}{51,8 - j0,0060 + (50 + j30) \left(\frac{\tanh(0,00192x25) + j \tanh(0,033x25)}{1 + j \tanh(0,00192x25) \tanh(0,033x25)} \right)} \\
&= (51,8 - j0,0060) \frac{50 + j30 + (51,8 - j0,0060)(0,104 + j1,080)}{51,8 - j0,0060 + (50 + j30)(0,104 + j1,080)} \\
&= (51,8 - j0,0060) \frac{55,39 + j85,94}{24,6 + j57,11} = \mathbf{84,0 - j14,1\Omega = 85,17\angle -9,52^\circ \Omega}
\end{aligned}$$

Calculate I_{IN}

$$I_{IN} = \frac{V_{IN}}{Z_{IN}} = \frac{100\angle 0^\circ V}{85,17\angle -9,52^\circ \Omega} = \mathbf{1,17\angle 9,52^\circ A}$$

Solve V^+ and V^-

$$\begin{aligned}
V(z=0) &= V_{IN} = V^+ + V^- = 100V\angle 0^\circ \\
I(z=0) &= I_{IN} = \frac{V^+}{Z_0} - \frac{V^-}{Z_0} = 1,17\angle 9,52^\circ A
\end{aligned}$$

By substitution:

$$I_{IN} = \frac{100\angle 0^\circ - V^-}{51,89\angle -0,00662^\circ} - \frac{V^-}{51,89\angle -0,00662^\circ} = 1,17\angle 9,52^\circ A \Rightarrow$$

$$V^- = \frac{100\angle 0^\circ - 60,71\angle 9,53^\circ}{2} = \mathbf{20,68\angle -14,06^\circ V = 20,06 - j5,03 V}$$

$$V^+ = 100\angle 0^\circ - 20,68\angle -14,06^\circ = 79,94 + j5,02 = \mathbf{80,09\angle +3,60^\circ V}$$

Voltage at load ($z=l$)

$$V(z=l) = V_L = V^+ e^{(-\gamma l)} + V^- e^{(\gamma l)}$$

$$\begin{aligned}
V_L &= V^+ e^{-(\alpha l + j\beta l)} + V^- e^{\alpha l + j\beta l} = V^+ e^{-\alpha l} e^{-j\beta l} + V^- e^{\alpha l} e^{j\beta l} \\
&= V^+ e^{-\alpha l} (\cos \beta l - i \sin \beta l) + V^- e^{\alpha l} (\cos \beta l + i \sin \beta l) \\
&= (79,94 + j5,02) e^{-0,00192x25} (\cos(0,033x25) - i \sin(0,033x25)) \\
&\quad + (20,06 - j5,03) e^{0,00192x25} (\cos(0,033x25) + i \sin(0,033x25)) \\
&= (79,94 + j5,02) x 0,953 x (0,679 - j0,735) + (20,06 - j5,03) x 1,049 x (0,679 + j0,735) \\
&= 73,41 - j40,86 V = \mathbf{84,01\angle -0,51^\circ V}
\end{aligned}$$

Current at load ($z=l$)

$$I(z=l) = I_L = \frac{V^+}{Z_0} e^{(-\gamma l)} - \frac{V^-}{Z_0} e^{(\gamma l)}$$

$$\begin{aligned}
I_L &= \frac{V^+ e^{-\alpha l} (\cos \beta l - i \sin \beta l)}{Z_0} - \frac{V^- e^{\alpha l} (\cos \beta l + i \sin \beta l)}{Z_0} \\
&= \frac{(79,94 + j5,02) * 0,953 * (0,679 - j0,735)}{51,88 - j0,0060} - \frac{(20,06 - j5,03) * 1,049 * (0,679 + j0,735)}{51,88 - j0,0060} \\
&= \frac{37,08 - j64,63}{51,88 - j0,0060} = 0,715 - j1,246 \text{ A} = \mathbf{1,44\angle -1,05^\circ \text{ A}}
\end{aligned}$$

Voltage at an arbitrary point (z') along the transmission line can be obtained (e.g. 10m from load)

$$V(z') = I_L [Z_L \cosh(\gamma z') + Z_0 \sinh(\gamma z')]$$

Because


$$\cosh(a + jb) = \cosh(a)\cos(b) + j\sinh(a)\sin(b)$$

and

$$\sinh(a + jb) = \sinh(a)\cos(b) + jcosh(a)\sin(b)$$

$$\begin{aligned}
V(z') &= I_L [Z_L [\cosh(\alpha z') \cos(\beta z') + i\sinh(\alpha z') \sin(\beta z')] \\
&\quad + Z_0 [\sinh(\alpha z') \cos(\beta z') + icosh(\alpha z') \sin(\beta z')]] \Rightarrow
\end{aligned}$$

$$\begin{aligned}
V(z' = 10) &= (0,715 - j1,246) [(50 + j30) [\cosh(0,0192) \cos(0,33) + i\sinh(0,019) \sin(0,33)] \\
&\quad + (51,88 - j0,006) [\sinh(0,0192) \cos(0,33) + icosh(0,0192) \sin(0,33)]] \\
&= (0,715 - j1,246) [(50 + j30)((0,946 + j0,006) + (51,88 - j0,006)(0,018 + j0,324))] \\
&= (0,715 - j1,246)(48,03 + j45,48) = -91,03 - j27,35 = \mathbf{95,05\angle -16,7^\circ \text{ V}}
\end{aligned}$$

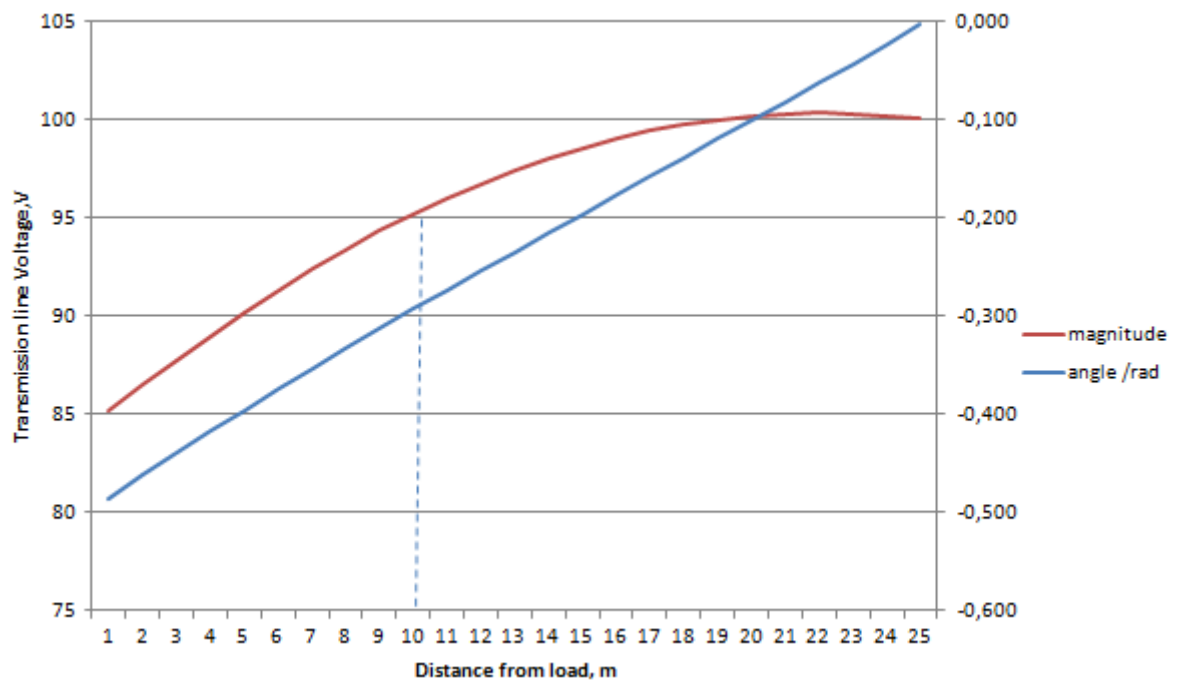

$$P_{avG} = \frac{1}{2} \text{Re}[V_G I_{IN}^*]$$

$$P_{avG} = \frac{1}{2} \text{Re}[V_G I_{IN}^*] = \frac{1}{2} \text{Re}[100 \angle 0^\circ (1,17 \angle 9,52^\circ)^*] = \frac{1}{2} \text{Re}[100 \angle 0^\circ (1,17 \angle -9,52^\circ)] W = 57,7 W$$

$$P_{avL} = \frac{1}{2} I_L^2 R_L$$

$$P_{avL} = \frac{1}{2} I_L^2 R_L = \frac{1}{2} 1,44^2 * 50 = \mathbf{51,8 W}$$

Voltage reflection coefficient at load is

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{(50 + j30) - (51,88 - j0,0060)}{(50 + j30) + (51,88 - j0,0060)} = 0,063 + j0,276 = \mathbf{0,283 \angle 77,17^\circ}$$


Voltage standing wave ratio is

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$


$$S = \frac{1 + 0,283}{1 - 0,283} = \mathbf{1,79}$$

7. Half-wave transmission line impedance transformer


A half-wavelength transmission line can be used as an impedance transformer. In this example the transmission line is assumed to be lossless.

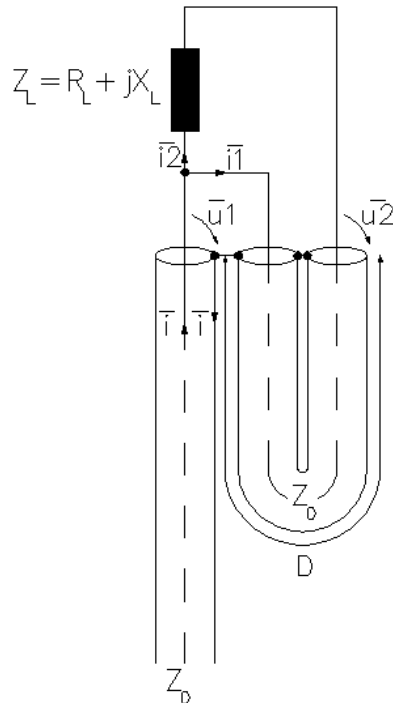

Kuva 10: Half-wavelength 1:4 impedance transformer

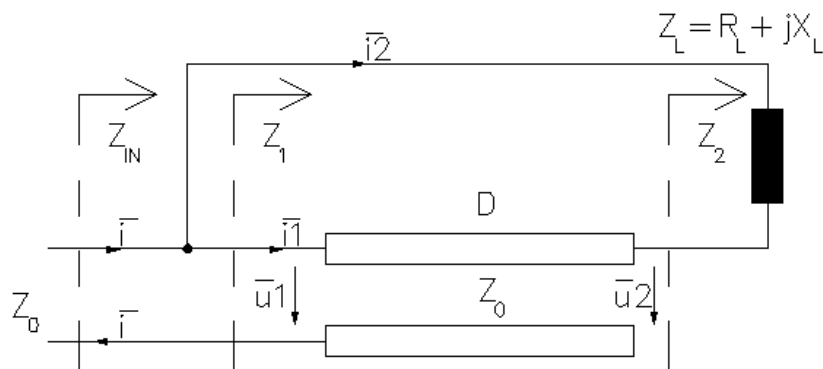

Kuva 11: Half-wavelength impedance transformer, schematic

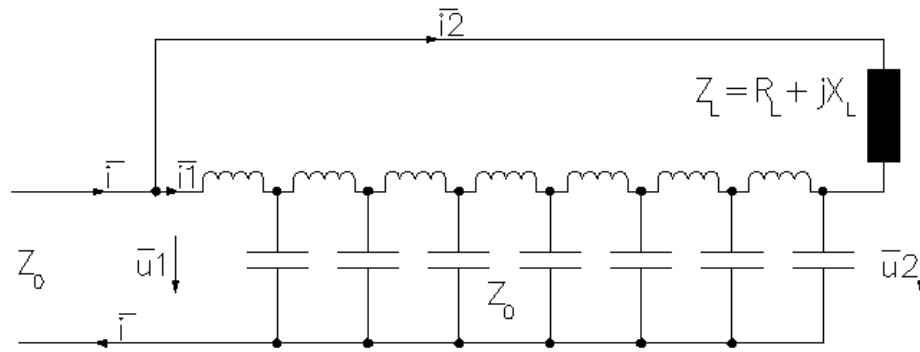


Kuva 12: Half-wavelength impedance transformer, lumped model

Load Z_L in this case is connected across the transmission line as shown in the schematic diagram. The resulting load impedance needed in the calculation of the transmission line input impedance Z_{IN} is therefore unknown, as it depends on the actual voltage u_2 and current i_2 at the end of the transmission line, which both depend on the resulting load impedance.

To be able to solve voltage and current along the transmission line an iterative method must be used.

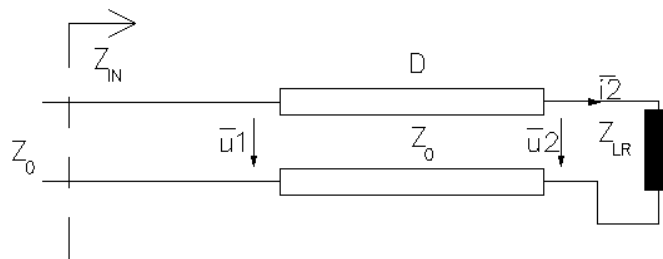1. Calculate Z_{IN} with an seed value (guess) of “reduced” load impedance Z_{LR}



$$Z_{IN} = Z_0 \frac{Z_{LR} + jZ_0 \tan \beta D}{Z_0 + jZ_{LR} \tan \beta D}$$

2. Calculate I_{IN}

$$I_{IN} = \frac{V_{IN}}{Z_{IN}}$$

3. Solve and calculate V^+ and V^-

$$V(0) = V^+ + V^-$$

$$I_{IN} = \frac{V^+}{Z_0} - \frac{V^-}{Z_0}$$

4. Calculate V and I at distance D (at the end of the transmission line)

$$V(D) = V^+ (\cos(-\beta D) + j \sin(-\beta D)) + V^- (\cos(\beta D) + j \sin(\beta D))$$

$$I(D) = \frac{V^+}{Z_0} (\cos(-\beta D) + j \sin(-\beta D)) - \frac{V^-}{Z_0} (\cos(\beta D) + j \sin(\beta D))$$


5. Calculate the current i_2 through actual load Z_L across the transmission line which would be caused by u_1 and $V(D)$

$$i_2 = \frac{u_1 - V(D)}{Z_L}$$

6. Calculate $-i_2$
7. Compare $-i_2$ with $I(D)$, both magnitude and phase shall match when “reduced” load impedance Z_{LR} is correct, if no match, change the initial reduced load impedance estimate and re-calculate.
8. When $-i_2$ and $I(D)$ match, voltage and current can be calculated at any point of the transmission line.

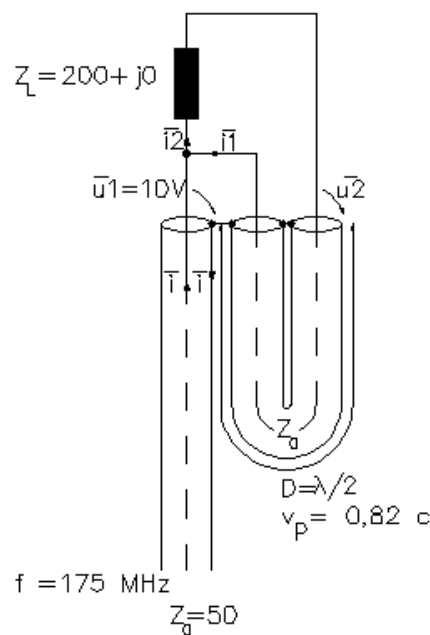7.1 Example

Define input impedance Z_{in} , voltage u_2 , currents i_1 and i_2 and voltage and current along the length of the $\lambda/2$ transmission line.



$$\beta = 2\pi/\lambda = 2\pi f/v_p = 2\pi 175 \cdot 10^6 / (0,82 \cdot 3 \cdot 10^8) = 4.4697 \text{ 1/m}$$

$$\beta D = (2\pi/\lambda) \cdot (\lambda/2) = \pi$$

Calculate Z_{IN} with a seed value (guess) of “reduced” load impedance $Z_{LR} = 70 + j0$ (arbitrary)

$$Z_{IN} = Z_0 \frac{Z_{LR} + jZ_0 \tan \beta D}{Z_0 + jZ_{LR} \tan \beta D} = 50 \frac{70 + j0 + j50 \tan \pi}{50 + j(70 + j0) \tan \pi} = 70 + j0$$

$$I_{IN} = \frac{V_{IN}}{Z_{IN}} = \frac{10 \angle 0}{70 \angle 0} = 0,14 \angle 0 \text{ A}$$

$$V^- = \frac{u_1 - (Z_0 * I_{IN})}{2} = \frac{10 \angle 0 - (50 * 0,14 \angle 0 \text{ A})}{2} = 1,429 \angle 0 \text{ V}$$

$$V^+ = u_1 - V^- = 10 \angle 0 - 1,429 \angle 0 \text{ V} = 8,571 \angle 0 \text{ V}$$

$$V(D) = V^+ (\cos(-\beta D) + j \sin(-\beta D)) + V^- (\cos(\beta D) + j \sin(\beta D))$$

$$= 8,571 \angle 0 \text{ V} (\cos(-\pi) + j \sin(-\pi)) + 1,429 \angle 0 \text{ V} (\cos(\pi) + j \sin(\pi)) = 10 \angle 180 \text{ V}$$

$$I(D) = \frac{V^+}{Z_0} (\cos(-\beta D) + j \sin(-\beta D)) - \frac{V^-}{Z_0} (\cos(\beta D) + j \sin(\beta D))$$

$$= \frac{8,571 \angle 0 \text{ V}}{50} (\cos(-\beta D) + j \sin(-\beta D)) - \frac{1,429 \angle 0 \text{ V}}{50} (\cos(\pi) + j \sin(\pi)) = 0,143 \angle 180 \text{ A}$$

$$i_2 = \frac{u_1 - V(D)}{Z_L} = \frac{10 \angle 0 - 10 \angle 180}{200 + j0} = 0,100 \angle 0$$

$$-i_2 = -0,100 \angle 0 = 0,100 \angle 180$$

$$I(D) = 0,143 \angle 180 \text{ A} \neq -i_2 = 0,100 \angle 180 \rightarrow$$

Make a new estimate for $Z_{LR} = 100 + j0$; do the calculation above again;

$$Z_{IN} = Z_0 \frac{Z_{LR} + jZ_0 \tan \beta D}{Z_0 + jZ_{LR} \tan \beta D} = 50 \frac{100 + j0 + j50 \tan \pi}{50 + j(100 + j0) \tan \pi} = 100 + j0$$

$$I_{IN} = i_1 = \frac{V_{IN}}{Z_{IN}} = \frac{10 \angle 0}{100 \angle 0} = 0,1 \angle 0 \text{ A}$$

$$V^- = \frac{u_1 - (Z_0 * I_{IN})}{2} = \frac{10 \angle 0 - (50 * 0,1 \angle 0 \text{ A})}{2} = 2,5 \angle 0 \text{ V}$$

$$V^+ = u_1 - V^- = 10 \angle 0 - 2,5 \angle 0 \text{ V} = 7,5 \angle 0 \text{ V}$$

$$V(D) = u_2 = V^+ (\cos(-\beta D) + j \sin(-\beta D)) + V^- (\cos(\beta D) + j \sin(\beta D))$$

$$= 7,5 \angle 0 \text{ V} (\cos(-\pi) + j \sin(-\pi)) + 2,5 \angle 0 \text{ V} (\cos(\pi) + j \sin(\pi)) = 10 \angle 180 \text{ V}$$

$$I(D) = \frac{V^+}{Z_0} (\cos(-\beta D) + j \sin(-\beta D)) - \frac{V^-}{Z_0} (\cos(\beta D) + j \sin(\beta D))$$

$$= \frac{7,5 \angle 0^\circ V}{50} (\cos(-\beta D) + j\sin(-\beta D)) - \frac{2,5 \angle 0^\circ V}{50} (\cos(\pi) + j\sin(\pi)) = 0,1 \angle 180^\circ A$$

$$i_2 = \frac{u_1 - V(D)}{Z_L} = \frac{10 \angle 0^\circ - 10 \angle 180^\circ}{200 + j0} = 0,1 \angle 0^\circ A$$

$$-i_2 = -0,1 \angle 0^\circ = 0,1 \angle 180^\circ$$


$$I(D) = 0,1 \angle 180^\circ A = -i_2, \text{ so } Z_{LR} \text{ is correct.}$$

$$i = I_1 + i_2 = 0,1 \angle 0^\circ A + 0,1 \angle 0^\circ = 0,2 \angle 0^\circ A$$


$$Z_{IN} = \frac{u_1}{i} = \frac{10 \angle 0^\circ V}{0,2 \angle 0^\circ A} = 50 \Omega$$

so $Z_{IN}/Z_L = 1/4$.

$V(D)$ and $I(D)$ can be calculated by varying D in the above formulas resulting in following distribution:

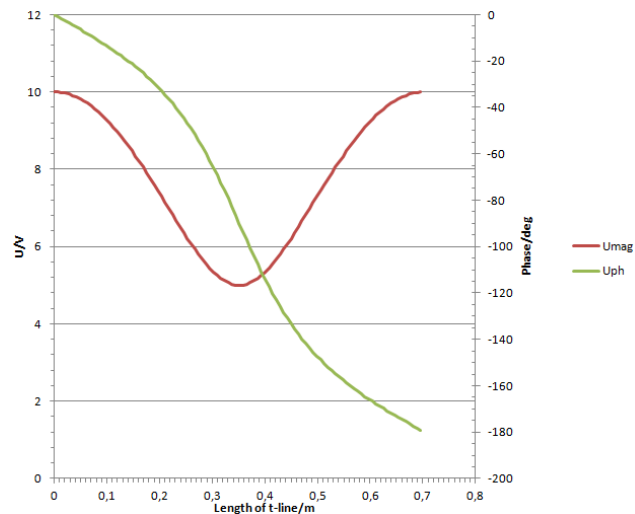

Kuva 13: Voltage along t-line

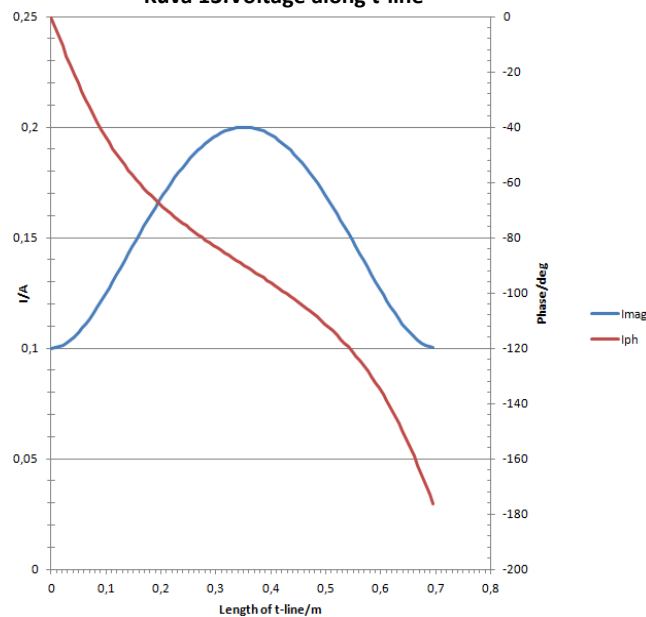

Kuva 14: Current along t-line