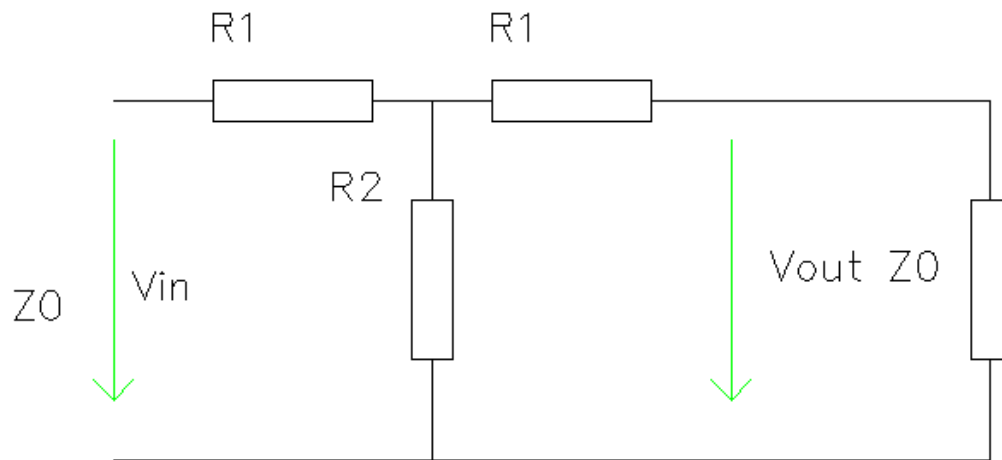


Deriving T-attenuator formulae



$$V_{OUT} = \frac{Z_0}{R_1 + Z_0} \frac{R_2 \parallel (R_1 + Z_0)}{R_1 + R_2 \parallel (R_1 + Z_0)} V_{IN} \quad (1)$$

$$A = \frac{V_{OUT}}{V_{IN}} = Z_0 \frac{R_2 \parallel (R_1 + Z_0)}{(R_1 + Z_0)(R_1 + R_2 \parallel (R_1 + Z_0))} \quad (2)$$

Because Input impedance of the attenuator must be equal to Z_0

$$R_1 + R_2 \parallel (R_1 + Z_0) = Z_0 \quad (3)$$

Substitute $R_2 \parallel (R_1 + Z_0) = Z_0 - R_1$ in (2)

$$A = Z_0 \frac{Z_0 - R_1}{(R_1 + Z_0)(R_1 + Z_0 - R_1)} = \frac{Z_0(Z_0 - R_1)}{Z_0(R_1 + Z_0)} \quad (4)$$

Solve R_1

$$AR_1 + AZ_0 = Z_0 - R_1 \rightarrow R_1 = Z_0 \frac{(1 - A)}{(1 + A)} \quad (5)$$

Write out the parallel impedance and substitute R_1 in (3)

$$\begin{aligned}
\frac{R_2(R_1 + Z_0)}{R_2 + (R_1 + Z_0)} &= Z_0 - R_1 \rightarrow \frac{R_2 \left(\left(Z_0 \frac{(1-A)}{(1+A)} \right) + Z_0 \right)}{R_2 + \left(\left(Z_0 \frac{(1-A)}{(1+A)} \right) + Z_0 \right)} = Z_0 - \left(Z_0 \frac{(1-A)}{(1+A)} \right) \rightarrow \\
\frac{\frac{R_2 Z_0 - R_2 Z_0 A}{(1+A)} + R_2 Z_0}{R_2 + \frac{Z_0(1+A)}{(1+A)} + Z_0} &= Z_0 \left(1 - \frac{(1-A)}{(1+A)} \right) \rightarrow \\
\frac{\frac{R_2 Z_0 - R_2 Z_0 A + R_2 Z_0 + R_2 Z_0 A}{(1+A)}}{R_2 + R_2 A + Z_0(1-A) + Z_0 + Z_0 A} &= Z_0 \left(1 - \frac{(1-A)}{(1+A)} \right) \rightarrow \\
\frac{2R_2 Z_0}{R_2(1+A) + 2Z_0} &= Z_0 \left(1 - \frac{(1-A)}{(1+A)} \right) \rightarrow \\
2R_2 &= [R_2(1+A) + 2Z_0] \left(1 - \frac{(1-A)}{(1+A)} \right) \\
&= R_2(1+A) - R_2(1-A) + 2Z_0 - 2Z_0 \frac{(1-A)}{(1+A)} \rightarrow \\
2R_2 &= 2R_2 A + 2Z_0 \frac{(1-A)}{(1+A)} \rightarrow R_2 = R_2 A + Z_0 \left(1 - \frac{(1-A)}{(1+A)} \right) \\
&= R_2 A + Z_0 \left(\frac{1+A-1+A}{1+A} \right) = R_2 A + Z_0 \left(\frac{2A}{1+A} \right) \rightarrow \\
R_2(1-A) &= 2Z_0 \frac{A}{(1+A)(1-A)} \rightarrow R_2 = 2Z_0 \frac{A}{(1-A^2)} \tag{6}
\end{aligned}$$